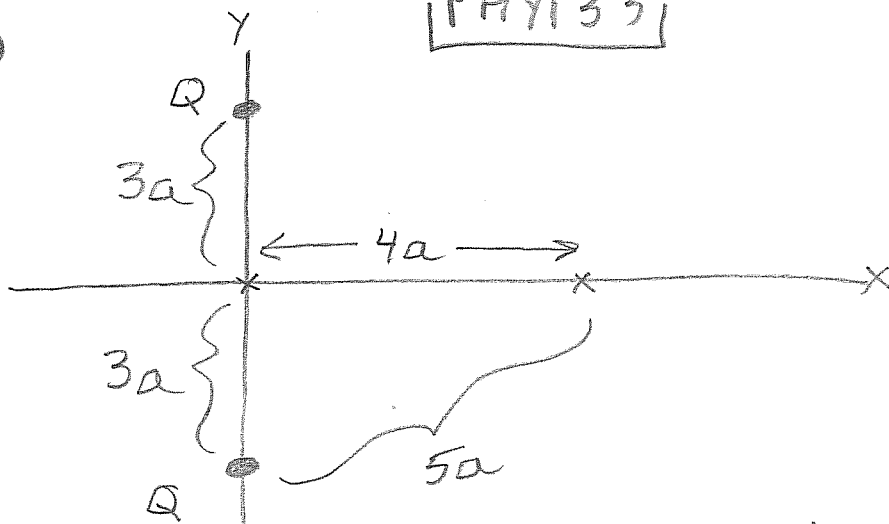


Solutions to Third Homework

PHY133

①




The electric potential at a position which is a distance r from a point source Q is $\frac{kQ}{r}$

$$\Delta V = \frac{kQ}{3a} + \frac{kQ}{3a} - \frac{kQ}{5a} - \frac{kQ}{5a}$$

$$\Delta V = \frac{kQ}{a} \left(\frac{2}{3} - \frac{2}{5} \right) = \boxed{\frac{4kQ}{15a}} \quad (-) \text{ is also OK}$$

②

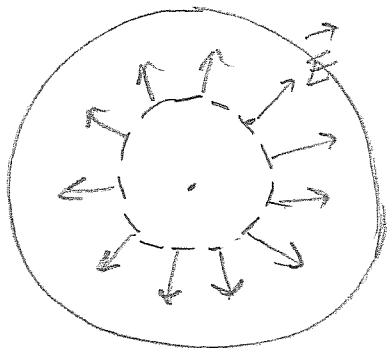

First use Gauss' Law to find \vec{E} inside the sphere. Since there is spherical symmetry, \vec{E} is radial and $|\vec{E}|$ only depends on r


$$\oiint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{inside}}}{\epsilon_0}$$

$$4\pi r^2 E = \frac{4}{3}\pi r^3 \rho / \epsilon_0$$

$$E = \frac{\rho r}{3\epsilon_0}$$

$$\Delta V = \int_0^R \frac{\rho r}{3\epsilon_0} dr = \frac{\rho r^2}{6\epsilon_0} \Big|_0^R = \boxed{\frac{\rho R^2}{6\epsilon_0}}$$

(3)

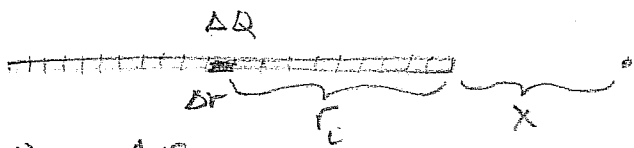

$$V_i = \frac{k\Delta Q}{r_i + x} = \frac{kQ \Delta r}{L(r_i + x)}$$

$$\frac{\Delta Q}{Q} = \frac{\Delta r}{L}$$


$$V = \sum V_i \rightarrow \int_0^L \frac{kQ}{L} \frac{dr}{(r+x)}$$

$$V = \frac{kQ}{L} (\ln(L+x) - \ln x)$$

$$E_x = -\frac{\partial V}{\partial x} = -\frac{kQ}{L} \left(\frac{1}{L+x} - \frac{1}{x} \right) = \frac{kQ}{x(L+x)}$$

In agreement with the result from lecture.

(4)

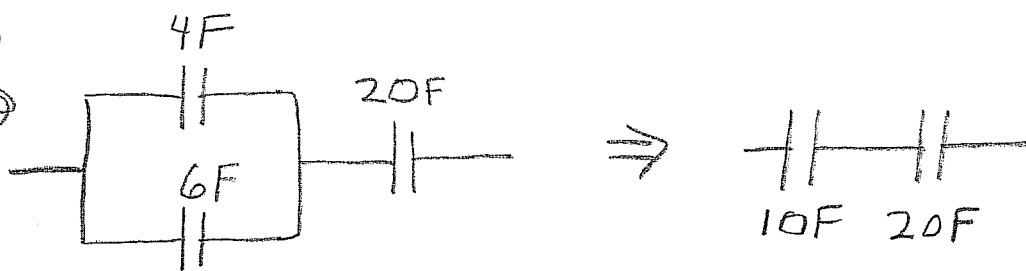

$$\frac{1}{C_{eq}} = \frac{1}{10} + \frac{1}{20} = \frac{3}{20}$$

$$C_{eq} = \frac{20}{3} F$$

$$Q = CV = \left(\frac{20}{3} \right) (12V) = 80 \text{ Coulombs on the } 20F \text{ capacitor}$$


$$V = \frac{Q}{C} = \frac{80}{20} = 4 \text{ Volts across the } 20F \text{ capacitor}$$

So there are $12 - 4 = 8$ Volts across both the 4F and 6F capacitors:

$$Q_4 = 8(4) = 32 \text{ Coulombs across the } 4F \text{ capacitor}$$

$$Q_6 = 8(6) = 48 \text{ Coulombs across the } 6F \text{ capacitor}$$

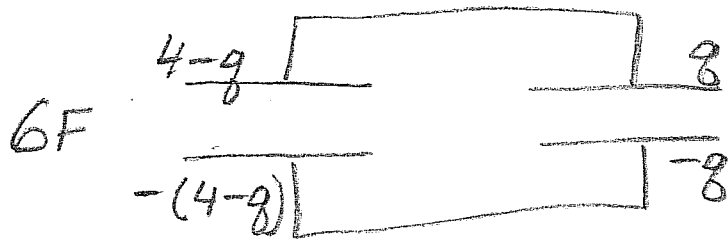(5) after the switch is closed, and the charges have come to equilibrium:



where q is charge that flows on the 9F capacitor.


Since the voltages are the same across the capacitors:

$$\frac{4-q}{6} = \frac{q}{9}$$

$$36 - 4q = 2q \Rightarrow \boxed{q = \frac{36}{6}} \text{ coulombs on the } 9F \text{ capacitor}$$

$$4 - q = \frac{24}{6} \text{ coulombs on the } 6F \text{ capacitor}$$


(6)

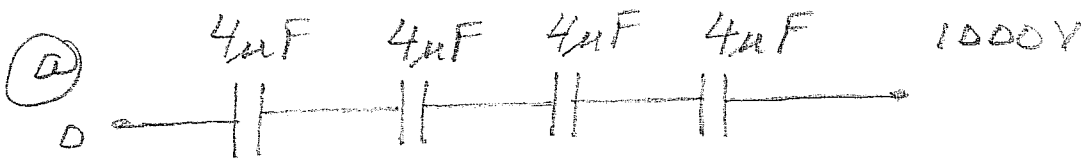


250V across each capacitor

$$\frac{1}{C_{\text{equiv}}} = \frac{1}{4} + \frac{1}{4} + \frac{1}{4} + \frac{1}{4} = 1$$
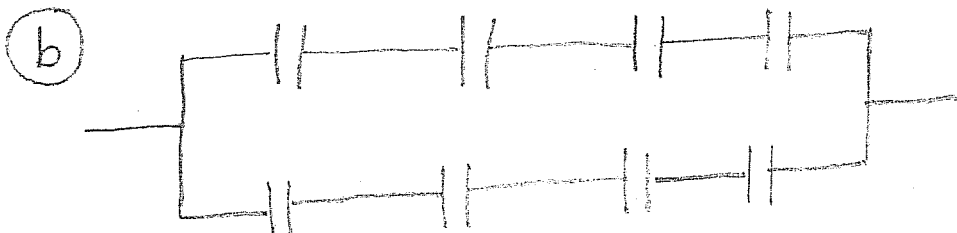
$$\Rightarrow C_{\text{equiv}} = 1 \mu F$$



$$C_{\text{equiv}} = 1 + 1 = 2 \mu F$$

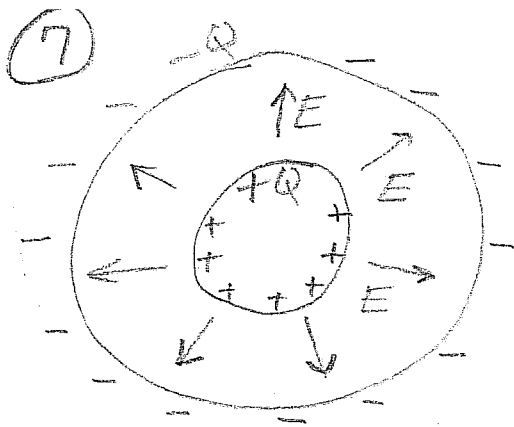

The electric field between the conductors is


$$|\vec{E}| = \frac{kQ}{r^2} \text{ and is radial.}$$

$$V = \int E dr = \int_a^b \frac{kQ}{r^2} dr$$


$$V = kQ \left(-\frac{1}{r}\right) \Big|_a^b = kQ \left(\frac{1}{a} - \frac{1}{b}\right) = \frac{kQ(b-a)}{ab}$$

$$\text{So } Q = \frac{ab}{k(b-a)} V \Rightarrow C = \frac{ab}{k(b-a)} = \boxed{\frac{4\pi\epsilon_0 ab}{b-a}}$$

⑧

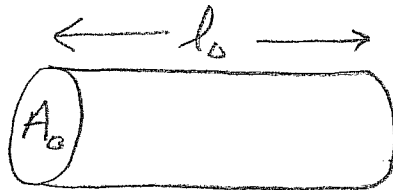

$$R = \frac{\rho l_0}{A_0}$$

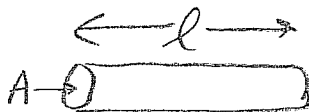

$$l = l_0/2$$

$$A = \pi \left(\frac{r_0}{2}\right)^2 = \frac{\pi r_0^2}{4} = \frac{A_0}{4}$$

$$\text{So New Resistance} = \frac{\rho l}{A} = \frac{\rho l_0/2}{(A_0/4)} = 2 \frac{\rho l_0}{A}$$

$$= \boxed{2R}$$