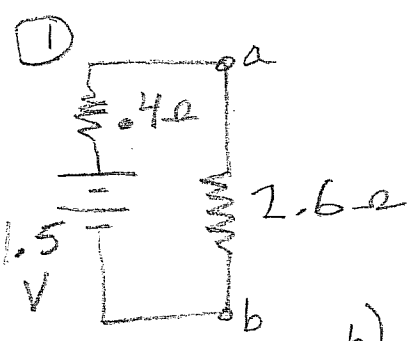


Solutions to Fourth Homework

PHY133




a) $R_{TOT} = .4 + 2.6 = 3 \Omega$

$I = \frac{V}{R} = \frac{1.5}{3} = \boxed{.5 \text{ A}}$

b) $V_{ab} = I(2.6 \Omega) = .5(2.6) = \boxed{1.3 \text{ V}}$


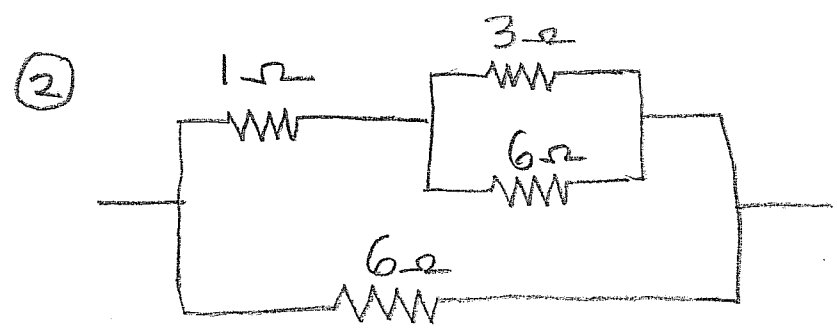
c) $1.4 \text{ amp-hr} = (.5 \text{ Amp})(x \text{ hours})$

$x = \frac{1.4 \text{ amp-hr}}{.5 \text{ amp}} = \boxed{2.8 \text{ hr}}$



$\frac{1}{3} + \frac{1}{6} = \frac{1}{2} = \frac{1}{R_{eq}}$

$R_{eq} = 2 \Omega$

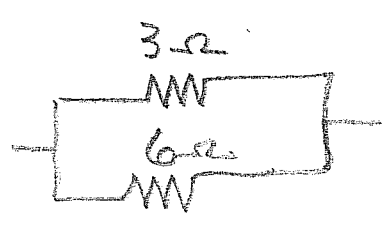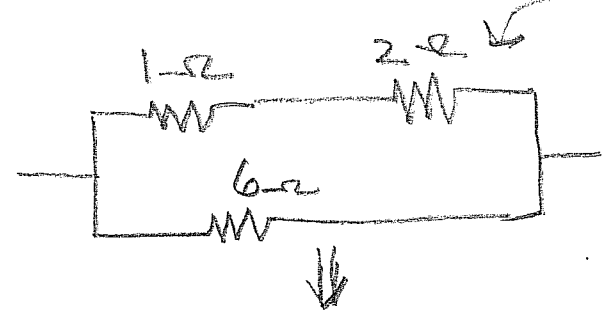

$\frac{1}{3} + \frac{1}{6} = \frac{1}{R_{TOT}}$

$\frac{1}{2} = \frac{1}{R_{TOT}} \Rightarrow$


$R_{TOT} = \boxed{2 \Omega}$

③ For 25 watts, the maximum current is

$$P = I^2 R$$

$$25 = I^2 (100\Omega) \Rightarrow I = \sqrt{\frac{25}{100}} = \underline{.5A}$$

So we must have

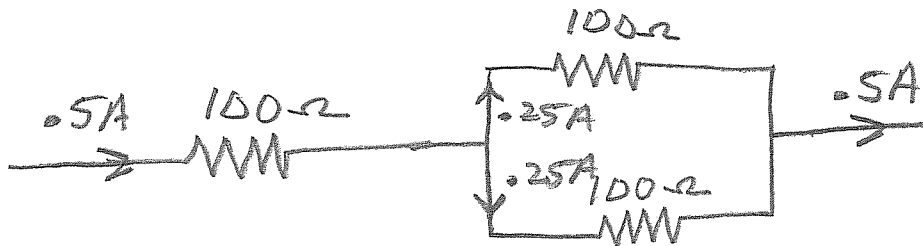


a) So the maximum voltage is

$$.5(100) + .25(100) = \boxed{75V}$$

b) TOTAL Power = $(.5)^2(100) + (.25)^2(100) + (.25)^2(100)$

$$= 25 + 6.25 + 6.25 = \boxed{37.5W}$$

④

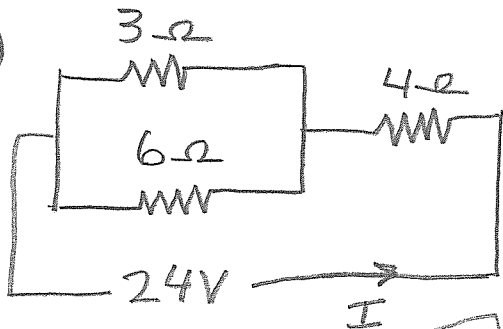

$$R_{TOT} = \frac{1}{\frac{1}{3} + \frac{1}{6}} + 4$$

$$R_{TOT} = 2 + 4 = 6\Omega$$

So $I = \frac{24}{6} = \boxed{4A}$ through the 4Ω resistor.


$V = 4(4) = \boxed{16 \text{ Volts}}$ across the 4Ω resistor

V across the 3Ω and 6Ω resistors = $24 - 16 = \boxed{8V}$

$$I_{\text{through } 3\Omega} = \frac{8V}{3\Omega} = \boxed{2\frac{2}{3}A}$$

$$I_{\text{through } 6\Omega} = \frac{8V}{6\Omega} = \boxed{1\frac{1}{3}A}$$

5

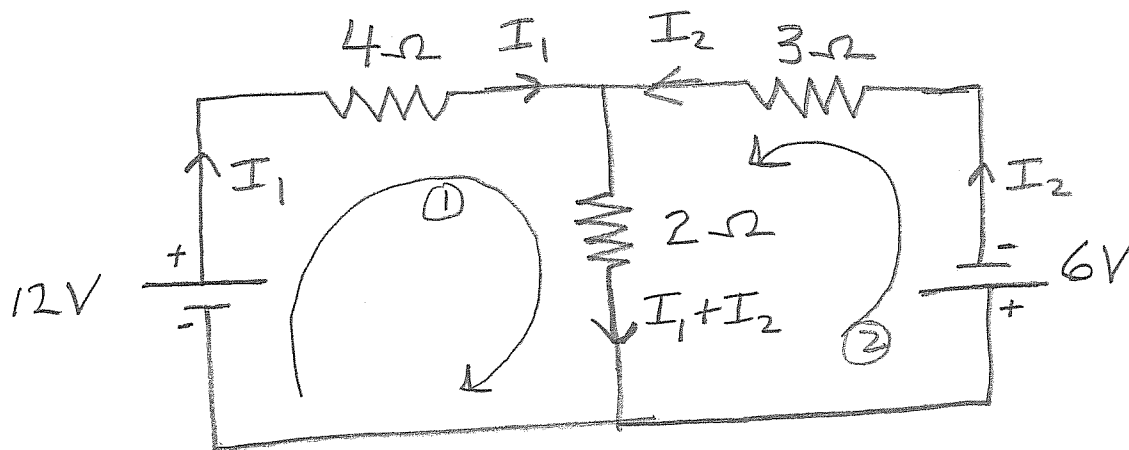

Loop 1: $+12 - 4I_1 - 2(I_1 + I_2) = 0$

$$12 = 6I_1 + 2I_2$$

① $\left[6 = 3I_1 + I_2 \right]$

Loop 2: $-6 - 3I_2 - 2(I_1 + I_2) = 0$

② $\left[-6 = +2I_1 + 5I_2 \right]$

Solving these equations:

$$5① - ② \Rightarrow 5(6) - (-6) = 5(3I_1) - 2I_1$$

$$36 = 13I_1$$


$$I_1 = \frac{36}{13} \text{ Amps}$$

$$6 = 3\left(\frac{36}{13}\right) + I_2$$

$$I_2 = 6 - 3\left(\frac{36}{13}\right) = -\frac{30}{13} \text{ Amps}$$

Through the 2Ω resistor flows $I_1 + I_2 = \frac{6}{13} \text{ Amps}$

6

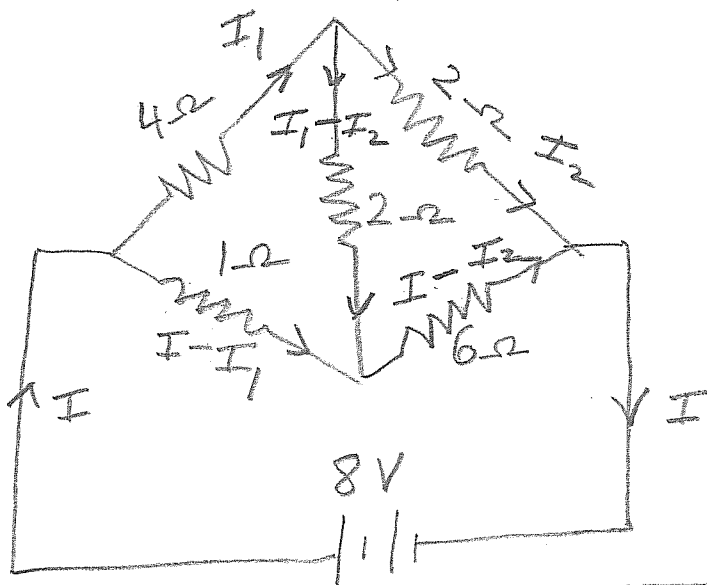

$$\begin{aligned}
 8 - 4I_1 - 2I_2 &= 0 \\
 8 - (I - I_1) - 6(I - I_2) &= 0 \\
 -4I_1 - 2(I_1 - I_2) + (I - I_1) &= 0
 \end{aligned}$$

$$\begin{aligned}
 4 &= 2I_1 + I_2 \\
 8 &= 7I - I_1 - 6I_2 \\
 0 &= I - 7I_1 + 2I_2
 \end{aligned}$$


a

$$I = \frac{\begin{vmatrix} 4 & 2 & 1 \\ 8 & -1 & -6 \\ 0 & -7 & 2 \end{vmatrix}}{\begin{vmatrix} 0 & 2 & 1 \\ 7 & -1 & -6 \\ 1 & -7 & 2 \end{vmatrix}} = \frac{4(-2-42) - 8(4+7)}{-7(4+7) + 1(-12+1)} = \boxed{3A}$$

b


$$R_{\text{effective}} = \frac{V}{I} = \frac{8}{3} = \boxed{2\frac{2}{3} \Omega}$$

7
a

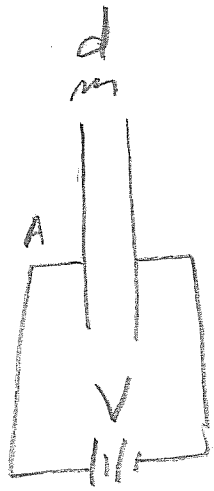

$$C_0 = \frac{\epsilon_0 A}{d}$$

$$U_0 = \frac{C_0 V^2}{2}$$

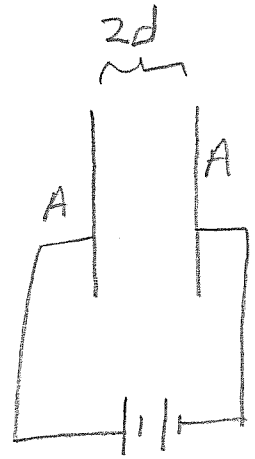

$$C = \frac{\epsilon_0 A}{2d}$$


$$C = \frac{C_0}{2}$$

$$U = (C_0/2) \frac{V^2}{2}$$

$$U = U_0/2$$


The energy decreases by a factor of 2

b

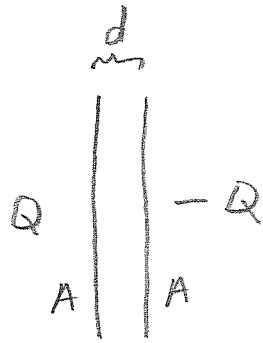

$$C_0 = \frac{\epsilon_0 A}{d}$$

$$U_0 = \frac{Q^2}{2C_0}$$

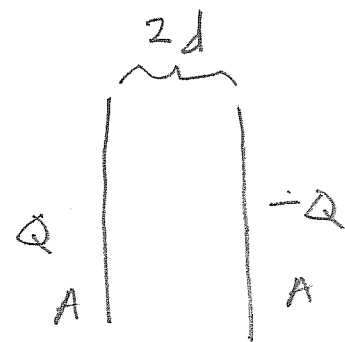



$$C = \frac{C_0}{2}$$

$$U = \frac{Q^2}{2(C_0/2)}$$

$$U = 2U_0$$

The energy increases by a factor of 2

8

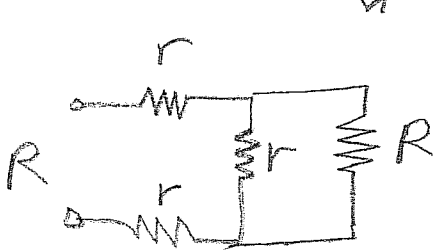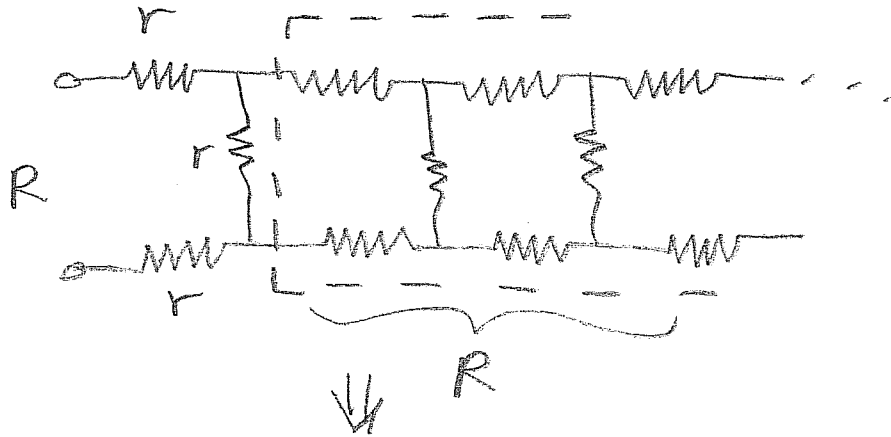

$$R = r + r + \frac{1}{\frac{1}{r} + \frac{1}{R}}$$

$$R = 2r + \frac{rR}{r+R}$$

$$R(r+R) = 2r(R+r) + rR$$

$$Rr + R^2 = 2rR + 2r^2 + rR$$

$$R^2 - 2rR - 2r^2 = 0$$

$$R = \frac{2r + \sqrt{4r^2 + 8r^2}}{2} = \boxed{r(1 + \sqrt{3})}$$

9

$$a) (.06 \text{ Kw})(12 \text{ hr}) \left(\frac{14¢}{\text{Kw-hr}} \right) = \boxed{10¢}$$

$$b) (1.5 \text{ Kw}) \left(\frac{1}{2} \text{ hr} \right) \left(\frac{14¢}{\text{Kw-hr}} \right) = \boxed{11¢}$$

$$c) (2 \text{ Kw})(8 \text{ hr}) \left(\frac{14¢}{\text{Kw-hr}} \right) = \boxed{\$2.24}$$

$$d) (.1 \text{ Kw})(8 \text{ hr}) \left(\frac{14¢}{\text{Kw-hr}} \right) = \boxed{11¢}$$