

Solutions to Hwr 1 PHY234

$$1) f = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

$$\sqrt{LC} = \frac{1}{2\pi f}$$

$$L = \left(\frac{1}{2\pi f}\right)^2 \frac{1}{C} = \left(\frac{1}{2\pi(10000)}\right)^2 \frac{1}{6.7 \times 10^{-6}}$$

$$L \approx 37.8 \mu\text{H}$$

2) With  $S_1$  closed, we have an RC circuit

$$\tau_c = RC \Rightarrow C = \frac{\tau_c}{R}$$

With  $S_2$  closed, we have an RL circuit


$$\tau_L = L/R \quad L = \tau_L R$$

With  $S_3$  closed, we have an LC circuit

$$T = \frac{2\pi}{\omega_0} = \frac{2\pi}{\frac{1}{\sqrt{LC}}} = 2\pi\sqrt{LC}$$

$$T = 2\pi\sqrt{(\tau_L R)\left(\frac{\tau_c}{R}\right)} = \boxed{2\pi\sqrt{\tau_L \tau_c}}$$


3) There are two combinations

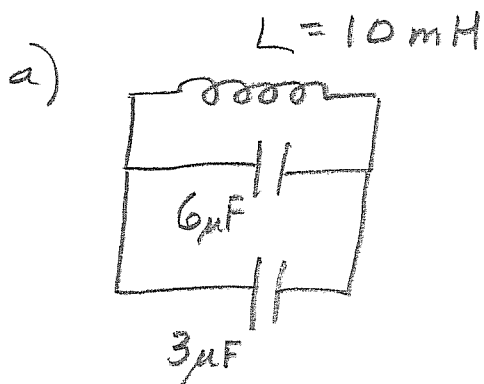

Here  $C_{\text{TOTAL}} = 9 \mu\text{F}$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$
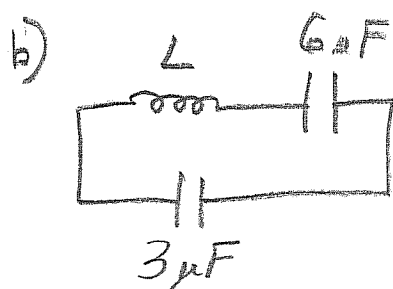
$$f_0 = \frac{1}{2\pi\sqrt{(10^{-2})(9 \times 10^{-6})}} \approx \boxed{530 \text{ Hz}}$$



Here  $\frac{1}{C_{\text{TOTAL}}} = \frac{1}{3} + \frac{1}{6} = \frac{1}{2}$

$$C_{\text{TOTAL}} = 2 \mu\text{F}$$

$$f_0 = \frac{1}{2\pi\sqrt{(10^{-2})(2 \times 10^{-6})}} \approx \boxed{1125 \text{ Hz}}$$

4) The charge on the capacitor in a LRC circuit is

$$Q(t) = A_0 e^{-\frac{R}{2L}t} \cos(\omega t + \phi)$$

If at  $t=0$ , the capacitor has its maximum charge,  $Q_0$ , then

$$Q(t) = Q_0 e^{-\frac{R}{2L}t} \cos(\omega t)$$

after one cycle,  $t=T$ , and the charge is

$$Q(T) = Q_0 e^{-\frac{RT}{2L}} \quad \text{since } \cos(\omega T) = 1$$

after 2 cycles, the charge on the capacitor is

$$Q(2T) = Q_0 e^{-\frac{R}{2L}(2T)}$$

$$\text{since } \cos(\omega 2T) = 1$$

after  $n$  cycles,

$$Q(nT) = Q_0 e^{-\frac{R}{2L}(nT)}$$

$$\text{since } \cos(\omega nT) = 1$$

The energy stored in a capacitor is

$$U = \frac{Q^2}{2C}$$

So from cycle  $n$  to  $n+1$  we have

$$\frac{\Delta U}{U} = \frac{\frac{Q_0^2 e^{-\frac{R}{L}nT}}{2C} - \frac{Q_0^2 e^{-\frac{R}{L}(n+1)T}}{2C}}{\frac{Q_0^2 e^{-\frac{R}{L}nT}}{2C}}$$

$$= 1 - e^{-\frac{RT}{L}}$$

$$\text{If } \frac{RT}{L} \ll 1 \quad e^{-\frac{RT}{L}} \approx 1 - \frac{RT}{L}$$

$$\text{So } \frac{\Delta U}{U} \approx \frac{RT}{L} = \frac{R}{L} \left( \frac{2\pi}{\omega} \right) = \frac{2\pi R}{\omega L}$$

⑤ a) at 1000 Hz,  $X_L = \omega L = L 2\pi f$

$$X_L = (.05 \text{ H}) 2\pi (1000) \approx 314 \Omega$$

$$I_m = \frac{V}{X_L} = \frac{30 \text{ V}}{314 \Omega} = \boxed{.095 \text{ A}}$$

⑥ b) at 8000 Hz  $X_L = (.05 \text{ H}) 2\pi (8000) = 2513 \Omega$

$$I_m = \frac{30 \text{ V}}{2513 \Omega} \approx \boxed{.012 \text{ A}}$$

⑥  $X_L = X_C$  when  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\text{so } f = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{(6 \times 10^{-3})(10^{-5})}}$$


$$\boxed{f \approx 650 \text{ Hz}}$$

⑦  $X_L = \omega_d L = 930 (2\pi) (.088) \approx 514 \Omega$

$$X_C = \frac{1}{\omega_d C} = \frac{1}{930 (2\pi) (.94 \times 10^{-6})} \approx 182 \Omega$$

$$X_L - X_C \approx 332 \Omega$$

$$\tan 75^\circ = \frac{332}{R}$$

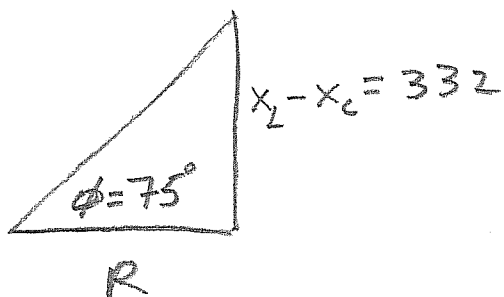


$$R = \frac{332}{\tan 75^\circ} \approx \boxed{90 \Omega}$$

⑧  $\omega_d = 60(2\pi) = 377 \text{ 1/s}$

let  $X_c = \frac{1}{\omega_d C}$

In position 2,  $|(X_L - X_c)| = \frac{120}{2} = 60 \Omega$

With the switch open, we have

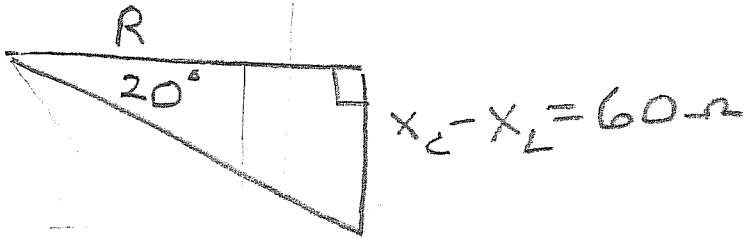


So,  $\frac{60}{R} = \tan 20^\circ \Rightarrow R = \frac{60}{\tan 20^\circ} \approx \boxed{165 \Omega}$

and  $X_c > X_L$  so  $\boxed{X_c = 60 + X_L}$

In position 1, the capacitive reactance is  $\frac{X_c}{2}$

So

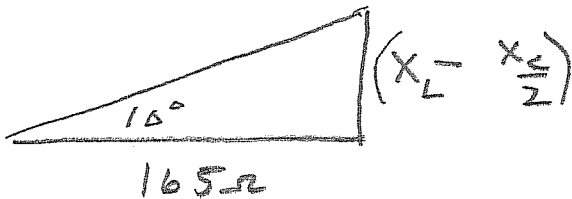

$\tan 10^\circ = \frac{X_L - \frac{X_c}{2}}{165}$

$X_L - \frac{X_c}{2} = 165 \tan 10^\circ$

$\boxed{X_L - \frac{X_c}{2} = 29 \Omega}$

Solving for  $X_c + X_L$

gives

$\frac{X_c}{2} = 60 + 29$

$\boxed{X_c = 178 \Omega}$   
 $\boxed{X_L = 118 \Omega}$


$C = \frac{1}{178(377)} \approx \boxed{14.9 \mu F}$

$L = \frac{118}{377} \approx \boxed{313 \text{ mH}}$

$$\textcircled{9} \quad X_C = \frac{1}{\omega C} = \frac{1}{2\pi(550)(4.7 \times 10^{-6})} \approx 61.6 \Omega$$

$$X_L = \omega L = 2\pi(550)(25 \times 10^{-3}) \approx 86.4 \Omega$$

⑩

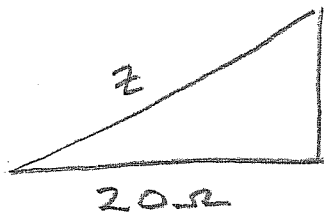

$$86.4 - 61.6 = 24.8$$


$$Z = \sqrt{20^2 + 24.8^2} \approx 31.9 \Omega$$

$$I_{RMS} \approx \frac{75V}{31.9 \Omega} \approx \boxed{2.35A}$$

$$\textcircled{b} \quad V_{ab} = R I_{RMS} = 15(2.35) \approx \boxed{35.3V}$$

$$\textcircled{c} \quad V_{bc} = X_C I_{RMS} = 61.6(2.35) \approx \boxed{145V}$$


$V_{cd}$ :

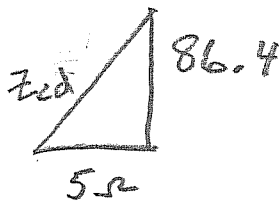

$$Z_{cd} = \sqrt{5^2 + 86.4^2} \approx 86.5 \Omega$$

$$V_{cd} = 86.5(2.35) \approx \boxed{203V}$$

$V_{bd}$ :

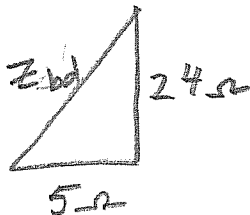


$$Z_{bd} = \sqrt{5^2 + 24^2}$$

$$Z_{bd} = 24.5 \Omega$$

$$V_{bd} = 24.5(2.35) \approx \boxed{57.6V}$$

$V_{ac}$ :

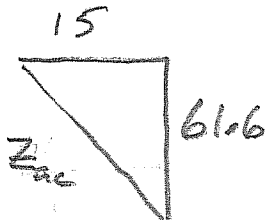

$$Z_{ac} = \sqrt{15^2 + 61.6^2} = 63.4 \Omega$$

$$V_{ac} = 63.4(2.35) \approx \boxed{149V}$$

(10)

For a parallel plate capacitor,

$$C = \frac{\epsilon_0 A}{d}$$

For a solenoid  $L = \frac{\mu_0 N^2 (\pi r^2)}{L} = \frac{\mu_0 \pi r^2 N^2}{L}$

So  $f_\Delta = \frac{\omega_\Delta}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$

$$f_\Delta = \frac{1}{2\pi\sqrt{\frac{\mu_0 \pi r^2 N^2}{L} \frac{\epsilon_0 A}{d}}}$$

$$= \frac{1}{2\pi} \sqrt{\frac{Ld}{(\epsilon_0 \mu_0) \pi r^2 N^2 A}}$$